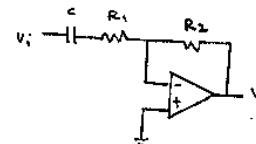


7. In the ideal op amp circuit, show that  $H = V_o/V_i = -R_2 / (R_1 + 1/j\omega C)$ .  
 If  $C = 1 \mu F$ ,  $R_1 = 2 k\Omega$  and  $R_2 = 10 k\Omega$ , find the magnitude of  $H$  ( $|H|$ ) when  $\omega = 0$ ,  $1/CR_1$  and  $\infty$ .  
 Hence sketch  $|H|$  versus  $\omega$ . What filter is it? (27)




$$\frac{V_o}{V_i} = 0 = \frac{0 - V_o}{Z_2}$$

$$\therefore \frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1 + \frac{1}{j\omega C}} \\ = H$$

6

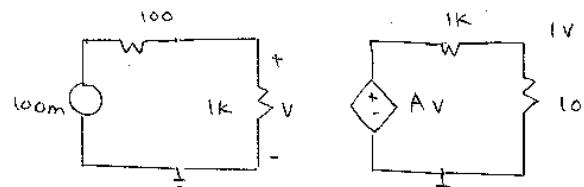5. A voltage amplifier (with voltage gain  $A$ , input resistance of  $1k\Omega$  and output resistance of  $1\Omega$ ) is used to amplify a  $100 \text{ mV}$  voltage source (with source resistance of  $100 \Omega$ ) to give a  $1\text{V}$  output to a  $10 \text{ k}\Omega$  load. Sketch the circuit model of the source-amplifier-load circuit and hence show that  $12.1$ . (16)




8

$$\therefore |A| = A_v \frac{10k}{11k}$$

$$= A \cdot 100m \frac{1k}{1.1k} \frac{10k}{11k}$$

8



$$\therefore A = 12.1$$

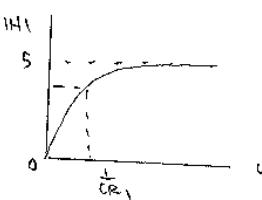

high pass  
filter


6

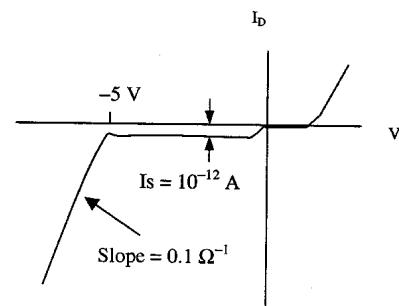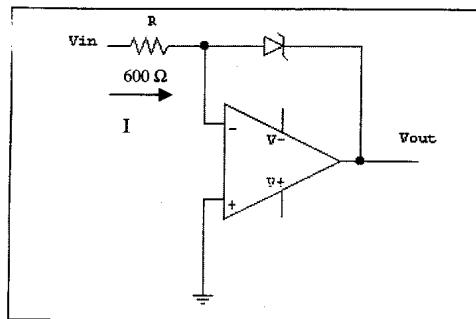7. Given the following circuit diagram, the input voltage  $V_{in}$  and the I-V characteristics of the zener diode.




$$\text{Diode equation : } I_D = I_s \exp\left(\frac{V_D}{26mV}\right)$$

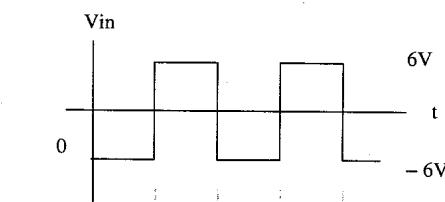
- a) Sketch the current I. Show your calculations clearly. (6 marks)  
 b) Sketch the output voltage  $V_{out}$ . Show your calculations clearly. (20 marks)


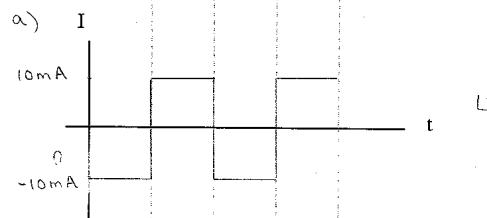
$$\begin{aligned} a) \quad I &= \frac{V_{in}}{R} \\ &= \frac{6V}{600} \\ &= 10 \text{ mA} \end{aligned}$$



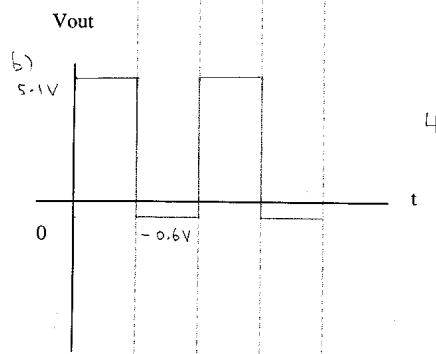
$$\begin{aligned} b) \quad I &= 10 \text{ mA} \\ \text{diode is forward biased} \\ I &= 10m = 1p e^{-\frac{V_0}{26m}} \end{aligned}$$




$$\begin{aligned} I &= -10 \text{ mA} \\ \text{diode is breakdown} \\ V_0 &= 5 + \frac{10m}{0.1} \\ &= 5.1 \text{ V} \end{aligned}$$

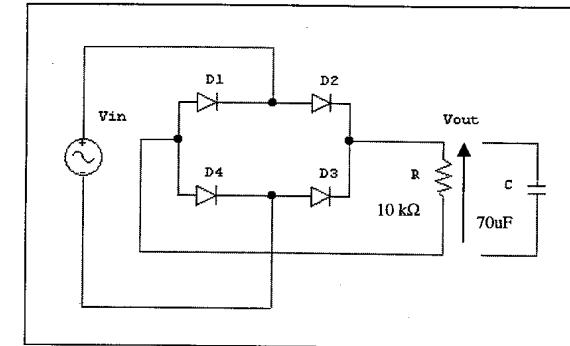8. Given the following ideal diode circuit diagram.



- a) Sketch the output voltage  $V_{out}$ . Show clearly the voltage and time intercepts. (5 marks)  
 b) Calculate the DC voltage  $V_{DC}$  across R ( $V_{DC} = 2Vm / \pi$ ). (3 marks)  
 c) Find the peak inverse voltage (PIV) of the diode. (4 marks)  
 d) Show that the ripple voltage  $V_r = 0.4V$  after a capacitor of  $70\mu\text{F}$  is connected across R. Justify the assumption that you used. (3 marks)  
 e) Estimate the DC voltage across R after the capacitor is added. (4 marks)

$V_{out}$

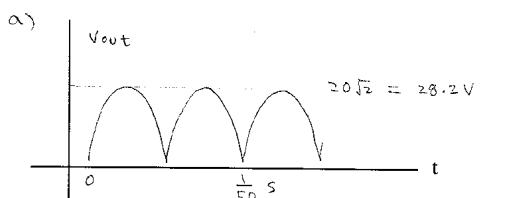

$$b) \quad V_{DC} = \frac{2Vm}{\pi} = \frac{2(28.2)}{\pi} = 18 \text{ V}$$



$$c) \quad \text{PIV} = V_m = 28.2 \text{ V}$$

$$d) \quad V_r = \frac{V_m}{2fRC} = \frac{28.2}{2(50)(10k)(70\mu\text{F})} = 0.4 \text{ V}$$


$$RC = 0.7 \text{ s} \gg \frac{1}{50} \text{ s} = \tau$$

$$e) \quad V_{DC} \approx V_m - \frac{V_r}{2} = 28.2 - 0.2 = 28 \text{ V}$$

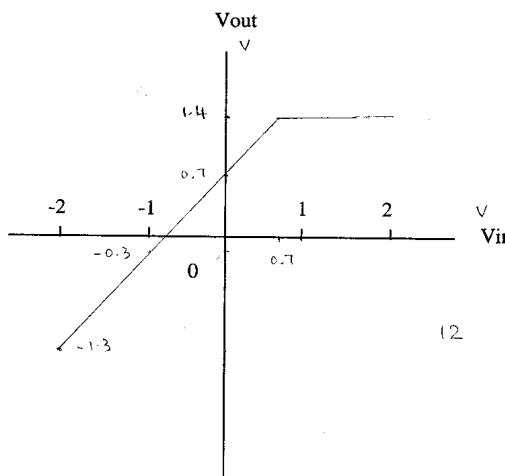
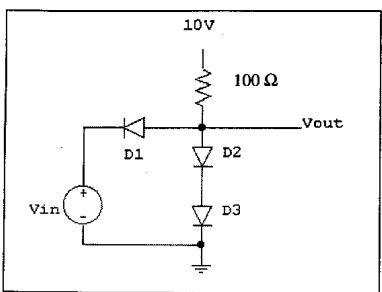
9. a) Plot the transfer curve  $V_{out}$  versus  $V_{in}$  for the following circuit ( $-2V \leq V_{in} \leq 2V$ ). Assume  $V_D = 0.7V$  when the diode is on. Show clearly the voltages. (12 marks)




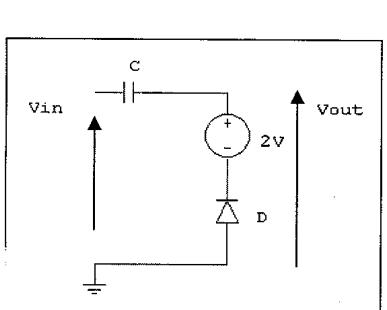
- b) Sketch  $V_{in}$  and  $V_{out}$  for the following circuit. Assume the diode is ideal. Show clearly the voltage and time intercepts. (12 marks)


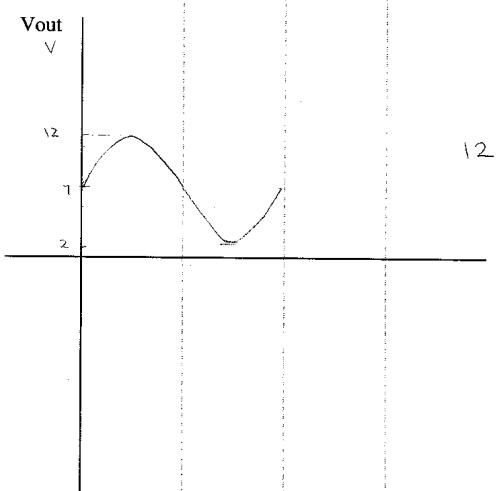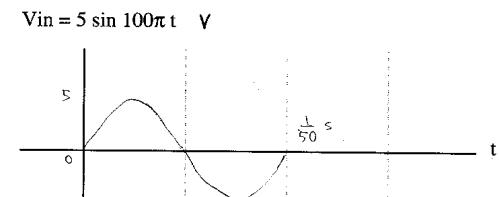
$$\begin{aligned}\omega &= 2\pi f \\ &\approx 100 \text{ rad/s} \\ \therefore f &= 50 \text{ Hz} \\ T &= \frac{1}{f} = 0.02 \text{ s}\end{aligned}$$



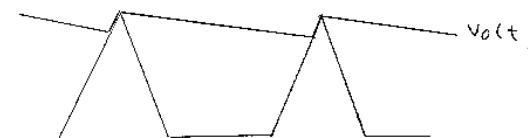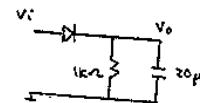9. In the ideal diode circuit,  $V_i$  is a 1 kHz triangular wave with 20V peak to peak (0V average).  
 (a) Sketch  $V_o(t)$ . (6)  
 (b) Show that the ripple voltage is roughly 0.5V. (8)  
 (c) Show also that the peak inverse voltage (PIV) of the diode is 20V. (4)



$$CR = 20 \mu F \cdot 1k \Omega = 20 \text{ ms}$$

$$\gg T = 1 \text{ ms}$$


$$\begin{aligned}\therefore V_r &= \frac{V_m T}{CR} = \frac{10 \text{ V} (1 \text{ ms})}{20 \text{ ms}} \\ &= 0.5 \text{ V}\end{aligned}$$

8

$$\text{PIV} = 2V_m = 20 \text{ V}$$

4

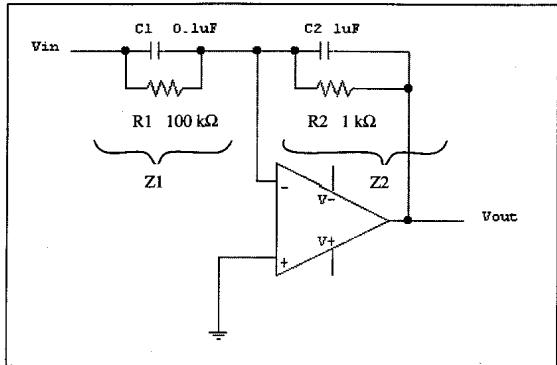11. Given the following circuit diagram. Assume ideal Op Amp.



a) Write the transfer function  $H(j\omega) = V_{out}(j\omega) / V_{in}(j\omega)$ . (10 marks)


Given :  $H = -Z_2 / Z_1$  for an inverting amp.

b) Show that  $|H(\omega)| = -40\text{dB}$  when  $\omega = 0$  and  $|H(\omega)| \approx -20\text{dB}$  when  $\omega = 10 / C_2 R_2$ . (12 marks)  
Appropriate assumption will be accepted.

c) Sketch the gain  $|H(\omega)|$  versus the frequency. (4 marks)

Given :  $|H(\omega)| \approx -23\text{dB}$  when  $\omega = 1 / C_2 R_2$  and  $|H(\omega)| \approx -37\text{dB}$  when  $\omega = 1 / C_1 R_1$ .

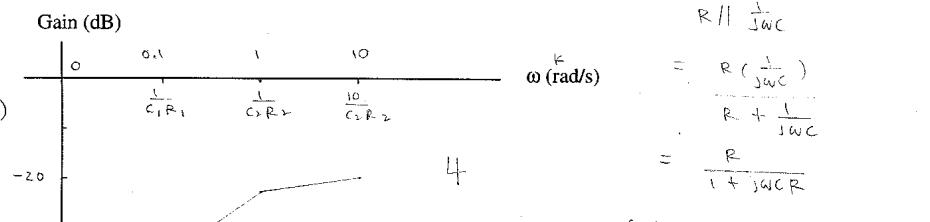d) What is the type of this filter? (2 marks)



$$C_1 R_1 = 0.1\mu(100k) = 10\text{mS}$$

$$C_2 R_2 = 1\mu(1k) = 1\text{mS}$$

$$\text{a) } H = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1 + j\omega C_1 R_1} = -\frac{R_2}{R_1} \frac{1 + j\omega C_1 R_1}{1 + j\omega C_2 R_2} \Big|_{10}$$



$$\text{b) } \omega = 0 \quad H = -\frac{R_2}{R_1} = -\frac{1k}{100k} \quad \text{or} \quad |H| = -40\text{dB}$$

$$\omega = \frac{10}{C_2 R_2} \quad H = -\frac{1}{100} \frac{1 + j\frac{10 C_1 R_1}{C_2 R_2}}{1 + j10} = -\frac{1}{100} \frac{1 + j10}{1 + j10}$$


$$\approx -\frac{1}{10} \quad \text{or} \quad |H| = -20\text{dB}$$

d) high pass filter

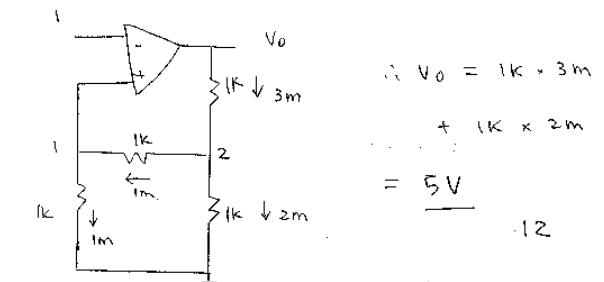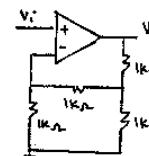6. (a) In the ideal op amp circuit, if  $V_i = 1\text{V}$ , find  $V_o$ . (12)




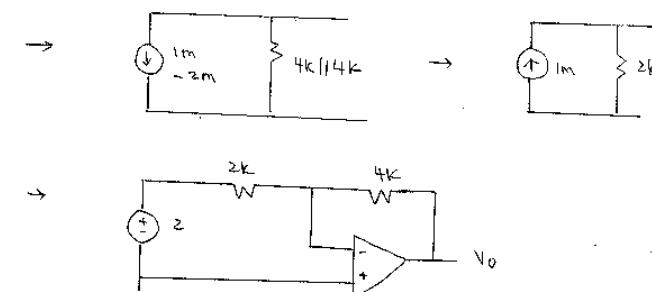(b) In the ideal op amp circuit, show that  $V_o = -4\text{V}$ . (Hint: use source transform). (16)



$$\therefore V_o = -\frac{4k}{2k} 2 = -4V \quad 4$$

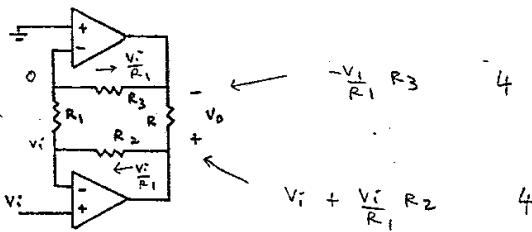8. For the following circuit, assume ideal op amp, show that  $V_o = V_i (1 + R_2/R_1 + R_3/R_1)$ . (20)



$$V_o = V_i \left(1 + \frac{R_2}{R_1}\right) - \left(-\frac{V_i R_3}{R_1}\right)$$

$$= V_i \left(1 + \frac{R_2}{R_1} + \frac{R_3}{R_1}\right)$$

$$R \approx \infty$$


$$A \ll R_1$$

can be a difference  
amp

9. Explain briefly the following real op amp properties: (i) input offset voltage, (ii) input bias current, (iii) slew rate. (9).



3



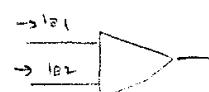


3

slew rate  $\sim$  maximum rate of change  
of  $V_o$



3

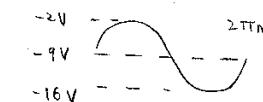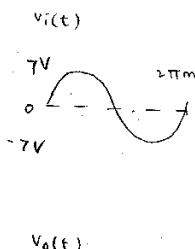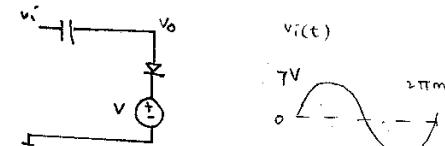6. (a) If  $V_i(t) = 7 \sin 1000t$  V and  $V = -2$  V, sketch  $V_i(t)$  and  $V_o(t)$  for the following ideal diode circuit. Show clearly the voltages and time in your sketch. (12)



12

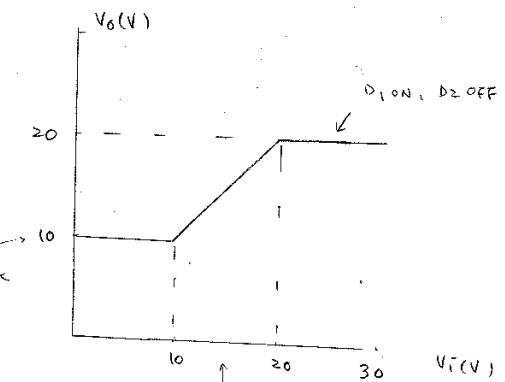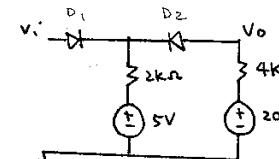(b) Plot  $V_o$  versus  $V_i$  for  $0V \leq V_i \leq 30V$  for the following ideal diode circuit. Show clearly all the voltages in your sketch. (13)



13


$$D_1 \text{ off}, D_2 \text{ on}$$

$$V_o = 5 + \frac{(20-5)2k}{2k+4k} \rightarrow 10$$

$$D_1 \text{ on}, D_2 \text{ on}$$

$$V_o = V_i$$

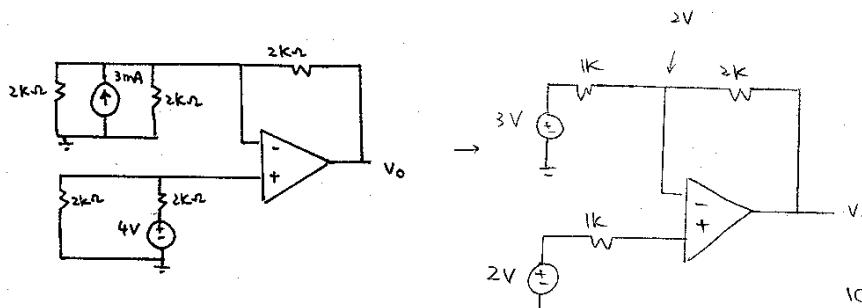8. (a) Find  $V_o$  for the following ideal op amp circuit. (14)




$$\therefore \frac{3 - 2}{1k} = \frac{2 - V_o}{2k}$$

$$\therefore V_o = 0V$$

4

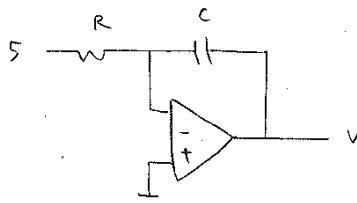(b) Design an ideal op amp circuit to obtain the solution of the following differential equation:

$$5 \frac{dv}{dt} + \frac{5}{7} = 0. \quad (14)$$



$$\frac{5}{R} = -C \frac{dv}{dt}$$



$$\therefore \frac{dv}{dt} + \frac{5}{CR} = 0$$

14

$$\text{Let } CR = 35 \quad \text{or} \quad R = 35k\Omega$$

$$C = 1mF$$

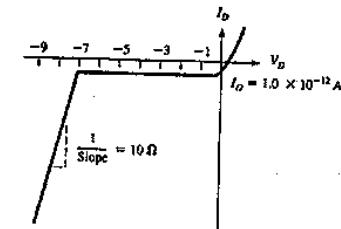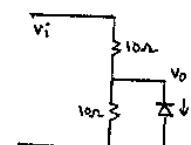10. In the following diode circuit, the diode has the reverse characteristics as shown.  
 (a) Find  $V_o$  and  $I$  if  $V_i = 4V$ . (9)  
 (b) Show that  $I = 0.2A$  if  $V_i = 20V$ . (17)



$$V_i = 4V$$


$$V_o = 2V$$

$$I = I_o = 1pA$$

5

4

$$V_i = 20V$$

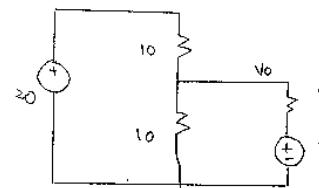

$$\therefore \frac{20 - V_o}{10} = \frac{V_o - 7}{10} + \frac{V_o}{10}$$

$$\therefore V_o = 9V$$

$$\therefore I = \frac{9 - 7}{10} = 0.2A$$

6

8

3