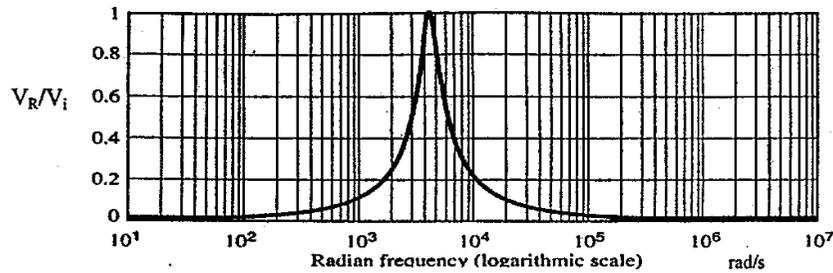


2. A series RLC circuit has the following magnitude plot.



- Estimate the resonant frequency. (2 marks)
- Estimate the bandwidth. (2 marks)
- Estimate the lower cut-off and higher cut-off frequencies. (4 marks)
- Calculate the Q factor. (3 marks)
- Calculate the value of the inductor if the value of the resistor is $1k\Omega$. (4 marks)
- Calculate the value of the capacitor. (4 marks)
- Calculate the power consumption at resonance if the input voltage $V_i(t) = 10\cos\omega t$ V. (5 marks)
- What is the ratio of V_c/V_i ? (2 marks)
- Calculate the resistance of another parallel RLC circuit that has the same magnitude plot. (6 marks)

a) $\omega_0 \sim 4.5k \text{ rad/s}$ 2

b) $BW \sim 2k \text{ rad/s}$ 2

c) $\omega_2 \sim 5.5k \text{ rad/s}$ 2

$\omega_1 \sim 3.5k \text{ rad/s}$ 2

d) $Q = \frac{\omega_0}{BW} = \frac{4.5k}{2k} = 2.25$ 3

e) $L = \frac{QR}{\omega_0} = \frac{2.25(1k)}{4.5k}$ 4
 $= 0.5H$

f) $C = \frac{1}{\omega_0^2 L} = \frac{1}{(4.5k)^2(0.5)}$ 4
 $= 0.1 \mu F$

g) $P = \frac{V^2}{R} = \left(\frac{10}{\sqrt{2}}\right)^2 \frac{1}{1k}$ 5
 $= \frac{1}{20} W$

h) $\frac{V_c}{V_i} = Q = 2.25$ 2


i) $R = Q\omega_0 L$ 6
 $= 2.25(4.5k)0.5$
 $= 5.06k\Omega$

4. Given a resistor (R), a capacitor (C) and an inductor (L).

- Show how to connect the resistor and the inductor to form a low-pass filter. Show the location of the output. (3 marks)
- Roughly sketch the frequency response of the low-pass filter (magnitude plot only). (2 marks)
- Show the relation between the half-power voltage gain and the bandwidth in your sketch. (2 marks)
- What is the relation between the resistance and the inductance to obtain the cut-off frequency to be 10kHz? (4 marks)
- How to add a capacitor to your circuit shown in (a) so that it can still be a low-pass filter. (3 marks)
- Derive the transfer function according to your circuit shown in (e). (5 marks)



3

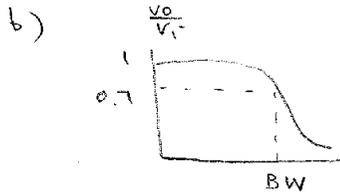


2

c) 2

d)
$$\omega = \frac{L}{R} = 2\pi f$$

$$= 2\pi (10K)$$

4

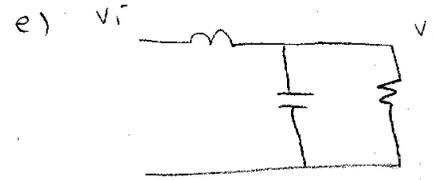

3


f)
$$\frac{v_o}{v_i} = \frac{R \parallel \frac{1}{j\omega C}}{j\omega L + R \parallel \frac{1}{j\omega C}}$$

$$= \frac{R}{1 + j\omega CR}$$

$$= \frac{1}{1 + \frac{1 + j\omega CR}{R} j\omega L}$$


5

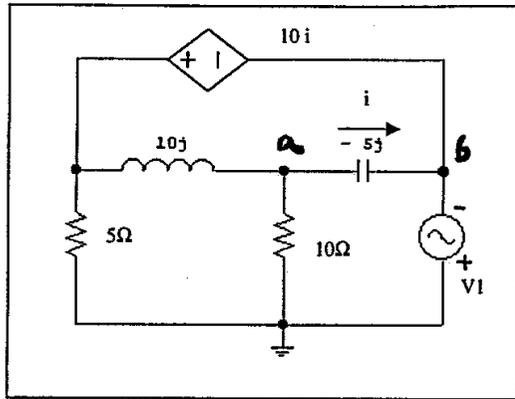5. Given : $V_1(t) = 10 \cos \omega t$ V.



at **ab**

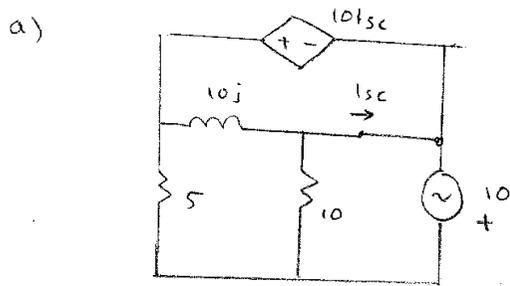
- Calculate I_{sc} . (10 marks)
- Calculate V_{oc} . (9 marks)
- Prove the total impedance $Z_{th} = V_{oc} / I_{sc} = 10j \Omega$. (3 marks)
- Calculate $i(t)$. (8 marks)
- Does $i(t)$ lead $V_1(t)$? (2 marks)



$$I_{sc} = \frac{10 I_{sc}}{10j} + \frac{10}{10}$$

$$\therefore I_{sc} = \frac{1}{1 - \frac{1}{j}} = \frac{1}{1+j}$$


10

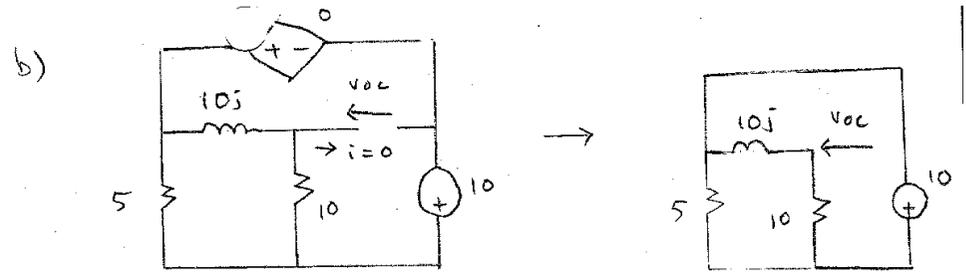

$$\begin{aligned} \therefore V_{oc} &= \frac{10j}{10 + 10j} \cdot 10 \\ &= \frac{10j}{1+j} \end{aligned}$$

9
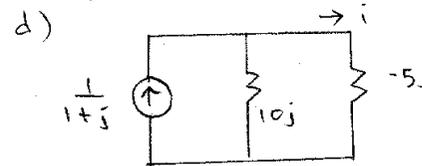
$$\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{10j}{\frac{1}{1+j}} = 10j \quad 3$$



$$\begin{aligned} \therefore i &= \frac{1}{1+j} \cdot \frac{10j}{10j - 5j} = \frac{2}{1+j} \\ &= \frac{2}{\sqrt{2} \angle 45} = \sqrt{2} \angle -45 \end{aligned}$$

6

$$\therefore i(t) = \sqrt{2} \cos(\omega t - 45^\circ) \text{ A}$$

2

e) $i(t)$ lags $v(t)$

2

END