

ELEC 101 BASIC ELECTRONICS

TEST 2 TIME: 1835 - 1955 08 November 1999 ANSWER ALL QUESTIONS


NOTE: Try your best to answer all questions. Write down clearly all work, steps, and formulae to get marks (marking will be based mainly on steps.) Total mark is 160 marks, i.e. 2 marks - 1 min work. So make best use of your time!

Name: \_\_\_\_\_ Department: \_\_\_\_\_

Student ID: \_\_\_\_\_ Email address: \_\_\_\_\_

Question	Q1	Q2	Q3	Q4	Q5	Total
Mark	(23)	(40)	(29)	(33)	(35)	(160)
		45				165

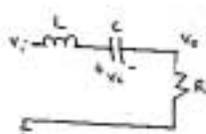1. In the series LCR circuit,  $L = 25\text{mH}$ ,  $C = 10\ \mu\text{F}$  and  $R = 1\ \Omega$ . (a) Find the frequency (in rad/s) of  $V_i$  such that (i)  $V_o = 0$ , (ii)  $V_o = V_i$ . (b) If the circuit is at resonance, find the Q factor. Find  $V_c$  if  $V_i = 1\text{V rms}$ . (c) If  $L$  is changed to  $50\ \text{mH}$  and  $R$  to  $2\ \Omega$ , find the bandwidth. (23)



(a) (i)  $V_o = 0$   $\omega = 0$  3

(ii)  $V_o = V_i$   $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$   
 $= \frac{1}{\sqrt{25\text{m} \cdot 10\ \mu}} = 2\text{k rad/s}$  5

(b)  $Q = \frac{\omega_0 L}{R} = \frac{2\text{k} \cdot 25\text{m}}{1} = 50$  5

$V_c = 50\text{V rms}$  5

(c)  $\text{BW} = \frac{\omega_0}{Q} = \frac{2}{50} = 40\ \text{rad/s}$  5

Power  $P = 24.2\text{kW}$ .

2. Three loads A, B and C are connected in parallel to a  $220\ \angle 0^\circ\ \text{V rms}$   $50\text{Hz}$  supply. Load A consumes  $50\ \text{kVAR}$  lagging with power factor (PF) of 0, load B consumes  $50\ \text{kW}$  at a PF of 0.5 leading, and load C is a  $1\ \Omega$  resistor in series with a  $1/100\pi\ \text{H}$  inductor. (a) Find the apparent power, reactive power, average power and PF of the combined load. (b) Find the element and value of load A. (c) Find the source current  $I_s(t)$  supplied to the combined load. (40)

load C:  $\frac{1}{j\omega L} = \frac{1}{j(2\pi 50) \frac{1}{100\pi}} = -j$

$\therefore Z = 1 + j = \sqrt{2} \angle 45^\circ$   $\therefore I = \frac{220 \angle 0}{\sqrt{2} \angle 45} = \frac{220}{\sqrt{2}} \angle -45^\circ\ \text{A rms}$

$\therefore P = I^2 R = \left(\frac{220}{\sqrt{2}}\right)^2 = 24.2\text{kW}$  12

$\therefore Q = I^2 X = \left(\frac{220}{\sqrt{2}}\right)^2 = 24.2\text{kVAR}$

$\therefore P = 0 + 50\text{kW} + 24.2\text{kW} = 74.2\text{kW}$  5

$Q = 50\text{k} - 50\text{k} \tan(\cos^{-1} 0.5) + 24.2\text{k}$   
 $= 12.4\text{kVAR}$  7

$\therefore S = \sqrt{74.2^2 + 12.4^2} = 75.2\text{kVA}$  4


$\text{PF} = \frac{P}{S} = \frac{74.2}{75.2} = 0.987$  lagging 5

load A:  $50\text{k} = \frac{V^2}{\omega L} = \frac{220^2}{2\pi 50 L}$  6


$\therefore L = 3\text{mH}$

$I_s(t) = \frac{75.2\text{k}}{220} \sqrt{2} \cos(2\pi 50t - \cos^{-1} 0.987)\ \text{A}$  6

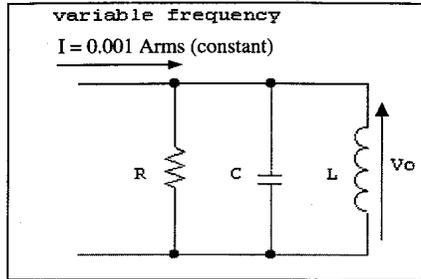1. The parallel RLC circuit shown below has a resonant frequency ( $\omega_0$ ) of 120k rad/s, a Q factor of 120 and a maximum  $V_o$  of 6 Vrms.



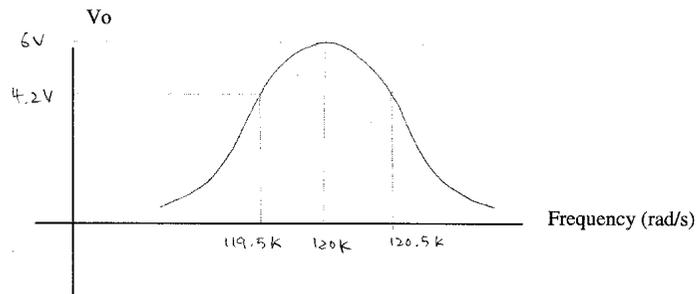- a) Find the bandwidth. (4 marks)  
 b) Sketch  $V_o$  versus frequency. Show the voltage at  $\omega_0$  and at the bandwidth in your sketch. (6 marks)  
 c) Find the values of R, L and C. (14 marks)



$$a) BW = \frac{\omega_0}{Q} = \frac{120k}{120} = 1k \text{ rad/s} \quad 4$$


$$c) R = \frac{6V}{1mA} = 6k \Omega \quad 4$$

$$L = \frac{R}{\omega_0 Q} = \frac{6k}{120k(120)} = 0.42mH \quad 5$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(120k)^2 \cdot 0.42m} = 167nF \quad 5$$

5. Given the following circuit diagram. Each load contains only one element.

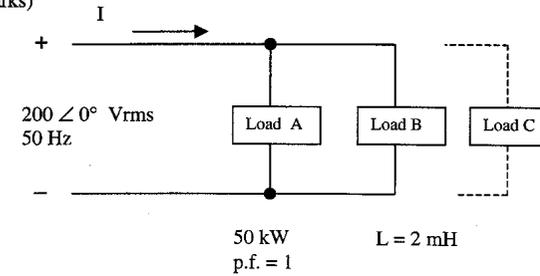- a) Determine the element and value of Load A. (5 marks)  
 b) Calculate the reactive power of Load B. (5 marks)  
 c) Calculate the total current I. (8 marks)  
 d) Calculate the power factor. Show lagging or leading. (5 marks)  
 e) If Load C is connected to improve the power factor to 1, calculate the reactive power of Load C. (5 marks)



$$a) A \text{ is } R$$

$$R = \frac{V^2}{P} = \frac{200^2}{50k} = 0.8 \Omega \quad 5$$

$$b) Q_B = \frac{V^2}{2\pi f L} = \frac{200^2}{2\pi(50)(2m)} = 63.7 \text{ kvar} \quad 5$$

$$c) I = \frac{200}{0.8} + \frac{200}{j(2\pi)(50)(2m)}$$


$$= 250 - 318j \text{ Arms} \quad 8$$

$$d) PF = \cos \theta = \cos \tan^{-1} \frac{63.7k}{50k}$$


$$= 0.62 \text{ lagging} \quad 5$$

$$e) Q_C = -63.7 \text{ kvar} \quad 5$$

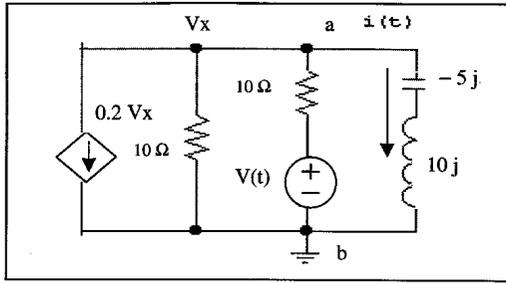6. Given :  $V(t) = 20 \cos \omega t$  V. Use Norton's Theorem to find the current  $i(t)$ .



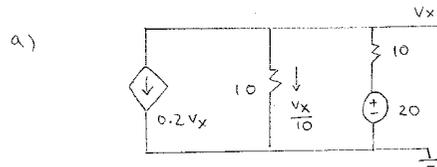- a) Find the open circuit voltage  $V_{oc}$  at terminals ab. (10 marks)
- b) Find the short circuit current  $I_{sc}$  at terminals ab. (7 marks)
- c) Show that the equivalent impedance  $Z_{th} = 2.5 \Omega$ . ( $Z_{th} = V_{oc} / I_{sc}$ ). (2 marks)
- d) Draw the Norton equivalent circuit of the whole circuit. (3 marks)
- e) Hence, find the current  $i(t)$ . (9 marks)
- f) Does  $i(t)$  lag  $V(t)$ ? (2 marks)




$$KCL = \frac{20 - V_x}{10} = \frac{V_x}{10} + 0.2 V_x$$

$$20 - V_x = V_x + 2 V_x$$

$$\therefore V_x = 5V = V_{oc}$$

10

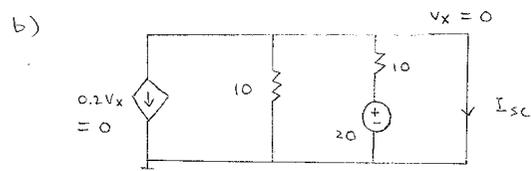


$$\therefore I_{sc} = \frac{20}{10} = 2A$$

7

$$c) Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{5V}{2A}$$

$$= 2.5 \Omega$$

2

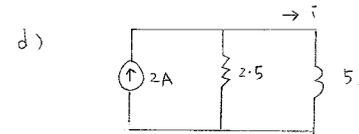

3

$$e) i = 2 \frac{2.5}{2.5 + 5j}$$

$$= \frac{1}{0.5 + j} = \frac{1}{\sqrt{1.25} \angle 63}$$

6


$$\therefore i(t) = 0.89 \cos(\omega t - 63^\circ) A$$

3

f)  $i(t)$  lags  $v(t)$

2

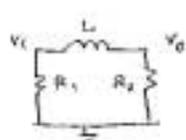3. In the following circuit, (a) find the complex transfer function  $H (= V_o/V_i)$  if  $R_1 = R_2 = 1\Omega$  and  $L = 1H$ . (b) Find the pole and zero of  $H$ . Find the frequency of  $V_i$  when (c) magnitude of  $V_o$  is one half the magnitude of  $V_i$ , and (d) phase of  $V_o$  is  $30^\circ$  lagging  $V_i$ . (e) What type of filter is the circuit? (f) Find the cut-off frequency if  $L$  is changed to  $2mH$ . (29)



$$(a) \quad \frac{V_o}{V_i} = \frac{R_2}{R_2 + j\omega L} = \frac{1}{1 + j\omega}$$

$$= \frac{1}{\sqrt{1 + \omega^2}} \angle -\tan^{-1}\omega$$

9

$$(c) \quad \frac{V_o}{V_i} = \frac{1}{2} = \frac{1}{\sqrt{1 + \omega^2}}$$

6

$$\therefore \omega = \sqrt{3} \text{ rad/s}$$

$$(d) \quad \theta = \tan^{-1}\omega = 30^\circ$$

6

$$\omega = \tan 30 = 0.577 \text{ rad/s}$$


(e) low pass filter

3

$$(f) \quad \omega_c = \frac{R}{L} = \frac{1}{2m} = 500 \text{ rad/s}$$

5

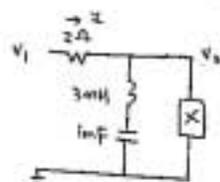5. In the following circuit,  $V_i(t) = 2 \cos(1000t - \pi/2)$  V. (a) If  $X$  is an open circuit, find  $V_2(t)$ . Find the element and value of  $X$  (b) if  $I = 0$ , (c) if  $V_1$  and  $I$  are in phase, and (d) if  $I$  leads  $V_1$  by  $45^\circ$ . (35)



$$= -2j$$

$$j\omega L = j(1k)(3m) = 3j$$

$$\frac{1}{j\omega C} = \frac{1}{j(1k)(1m)} = -j$$

$$(a) \quad \therefore V_2 = -2j \frac{2j}{2+2j} = \frac{2}{1+j}$$

$$= \sqrt{2} \angle -45^\circ$$

$$\therefore v_2(t) = \sqrt{2} \cos(1000t - \frac{\pi}{4}) \text{ V}$$

12

$$(b) \quad I = 0 \text{ if } X \parallel 2j = \infty = \frac{X(2j)}{X+2j}$$

8

$$\therefore X = -2j = \frac{-j}{\omega C}$$

$$\therefore C = \frac{1}{2\omega} = \frac{1}{2k} = 0.5mF$$

(c)  $V_1, I$  in phase if  $X = 0$

4

$$(d) \quad \frac{V(2j)}{X+2j} = -2j$$

11

$$\therefore X = -j$$

$$\therefore C = 1mF$$

End of paper. Good luck. Try the best and very good study!