

Electronic Circuits I
Dec., 15, 1998, 12:30pm - 3:30pm, G017
Examiner: Dr. Ki Wing-Hung

Name: Solin (English) Name: 蘇麟 (Chinese)
Student Number: _____ Signature: _____

Directions:

- (1) This is a closed book examination. No additional sheet is allowed.
- (2) Calculators are allowed.
- (3) Answer all questions in the space provided. Request for additional sheets from proctors only if necessary.
- (4) Show all your calculations. No marks will be given for unjustified answers.
- (5) Do your own work. Any form of cheating is a violation of academic integrity, and will be dealt with accordingly.



Question	Maximum Score	Score
1	12	
2	14	
3	8	
4	6	
5	8	
6	12	
7	20	
8	20	
Total	100	

The following equations are provided for your reference. Use them if needed.

Diode:	$I_d = I_s(e^{\frac{V_d}{V_T}} - 1)$	$I_s = 2 \times 10^{-15} \text{ A}, V_T = 25 \text{ mV}$
NMOS:	cutoff $V_{gs} < V_t$	
	linear $V_{gs} - V_t \lesssim V_{ds}$	$I_d = k_n[(V_{gs} - V_t)V_{ds} - \frac{1}{2}V_{ds}^2]$
	saturation $V_{gs} - V_t \gtrsim V_{ds}$	$I_d = \frac{1}{2}k_n(V_{gs} - V_t)^2$
PMOS:	cutoff $ V_{gs} < V_{tp} $	
	linear $ V_{gs} - V_{tp} \lesssim V_{ds} $	$ I_d = k_p[(V_{gs} - V_{tp}) V_{ds} - \frac{1}{2} V_{ds} ^2]$
	saturation $ V_{gs} - V_{tp} \gtrsim V_{ds} $	$ I_d = \frac{1}{2}k_p(V_{gs} - V_{tp})^2$

1

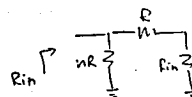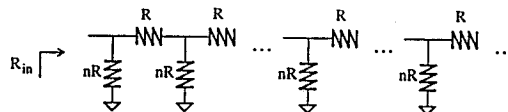- 1a) Given an infinite resistive ladder network as shown below. Calculate the input resistance R_{in} if $n = 6$ and $R = 1 \text{ k}\Omega$. (Hint: Any interesting observation when the array is infinite?) 6 marks



$$R_{in} = nR // (R + R_{in}) = \frac{nR(R + R_{in})}{nR + R + R_{in}}$$

$$\Rightarrow nR R_{in} + R R_{in} + R^2 = nR^2 + nR R_{in}$$

$$\Rightarrow R^2 + R R_{in} - nR^2 = 0$$

$$\Rightarrow R_{in} = \frac{-R \pm \sqrt{R^2 + 4nR^2}}{2}$$


$$= \frac{\sqrt{4n+1} - 1}{2} R$$

$$= \frac{\sqrt{4 \cdot 6 + 1} - 1}{2} 1 \text{ k}$$

$$= 2 \text{ k} \Omega$$

2

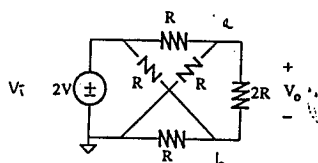- b) Calculate the output voltage of the following lattice network. 6 marks
(Hint: Use nodal analysis. Do not use $\Delta \leftrightarrow Y$ transformation. The "cross" is not connected.)



$$a) \frac{V_i - V_a}{R} = \frac{V_a - V_b}{2R} + \frac{V_a}{R}$$

$$\Rightarrow 2V_i - 2V_a = V_a - V_b + 2V_a$$

$$\Rightarrow 5V_a - V_b = 2V_i \quad (1)$$

$$b) \frac{V_i - V_b}{R} + \frac{V_a - V_b}{2R} = \frac{V_b}{R}$$

$$\Rightarrow 2V_i - 2V_b + V_a - V_b = 2V_b$$

$$\Rightarrow -V_a + 5V_b = 2V_i \quad (2)$$

$$\Rightarrow 5V_a - V_b = 2V_i$$

$$-5V_a + 25V_b = 10V_i$$

$$24V_b = 12V_i$$

$$\Rightarrow V_b = \frac{1}{2}V_i$$


$$V_a = 5V_b - 2V_i = \frac{5}{2}V_i - 2V_i$$

$$= \frac{1}{2}V_i$$

$$V_o = V_a - V_b = 0$$

3

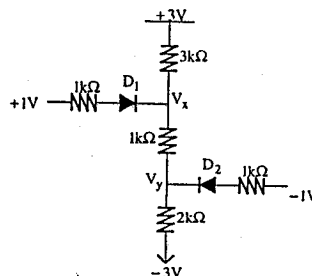- 2a) Calculate V_x and V_y of the following diode circuit. Assume all diodes are ideal. 6 marks



If +1V and -1V are not added, then

$$V_x' = 3 - 3 = 0 \text{ V}$$

$$V_y' = 2 - 3 = -1 \text{ V}$$

By adding +1V, D_1 will turn on. The added current increases V_y' , thus reverse biasing $D_2 \Rightarrow D_2$ off.

$$\therefore \frac{1 - V_x}{1 \text{ k}} + \frac{3 - V_x}{3 \text{ k}} = \frac{V_x - 3}{3 \text{ k}}$$

$$\Rightarrow 3 - 3V_x + 3 - V_x = V_x + 3$$


$$\Rightarrow 5V_x = 3 \Rightarrow V_x = \frac{3}{5} = 0.6 \text{ V}$$

$$V_y = \frac{2 \text{ k}}{1 \text{ k} + 2 \text{ k}} (V_x + 3) - 3 = \frac{2}{3} (\frac{3}{5} + 3) - 3$$


$$= \frac{2 \cdot 14}{3 \cdot 5} - 3 = 2.4 - 3 = -0.6 \text{ V}$$

4

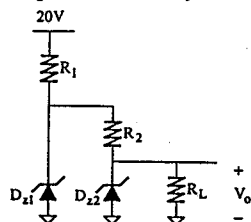- 2b) With the zener diode models as shown, compute V_o . (That is, each diode D_z is modeled as a battery in series with a resistor.) 8 marks


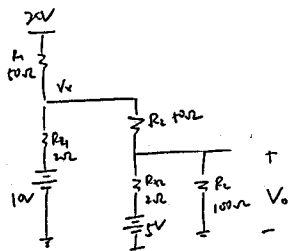
$$\begin{aligned} V_{z10} &= 10V \\ V_{z20} &= 5V \\ R_1 &= R_2 = 50\Omega \\ R_L &= 100\Omega \\ R_{z1} &= R_{z2} = 2\Omega \end{aligned}$$




$$\frac{20 - V_x}{50} = \frac{V_x - 10}{2} + \frac{V_x - V_0}{50} \Rightarrow 20 - V_x = 25V_x - 250 + V_x - V_0$$

$$\Rightarrow 270 = 24V_x - V_0 \quad (1)$$

$$\frac{V_x - V_0}{50} = \frac{V_0 - 5}{2} + \frac{V_0}{100} \Rightarrow 2V_x - 2V_0 = 50V_0 - 250 + V_0$$
$$\Rightarrow 2V_x = 53V_0 - 250 \quad \text{--- (2)}$$

$$\begin{aligned} \Rightarrow \text{in } \textcircled{1} \Rightarrow \quad 270 &= 27 \left(\frac{1}{2} V_0 - 125 \right) - V_0 \\ \Rightarrow 714.5 V_0 &= 3645 \\ V_0 &= 5.1 \text{ V} \end{aligned}$$

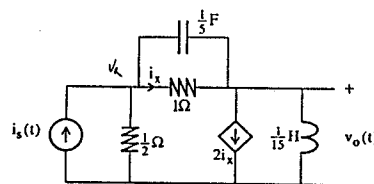- 3) Compute the output voltage of the circuit below that operates in the sinusoidal steady state. 8 marks




$$i_c(t) = 5 \cos(5t + 60^\circ)$$

$$\begin{aligned} \textcircled{2} V_A &= \bar{v}_s = \frac{V_A}{x} + \frac{V_A - V_0}{y + \frac{1}{2}} + \frac{V_A - V_0}{1} \\ \Rightarrow \bar{v}_s &= 2V_A + j(V_A - V_0) + V_A - V_0 \\ &= V_A(3 + j) - V_0(1 - j) \end{aligned} \quad \textcircled{1}$$

$$\begin{aligned} \textcircled{2} V_0 &= \frac{V_A - V_0}{\frac{1}{j}} + \frac{V_A - V_0}{1} = 2 \frac{V_A - V_0}{1} + \frac{V_0}{j \cdot \frac{1}{j}} \\ \Rightarrow jV_A - jV_0 + V_A - V_0 &= 2V_A - 2V_0 - j^3 V_0 \\ \Rightarrow V_A(2 - j) &= V_0(2 + j^3 - j - 1) \\ \Rightarrow V_A(1 - j) &= V_0(1 + j^2) \quad \text{--- (2)} \end{aligned}$$

$$\begin{aligned} \textcircled{2} \text{ in } \textcircled{1} \Rightarrow \quad \vec{E} &= \frac{1+j}{1-j} V_0 (3+j) - V_0 (1-j) \\ \Rightarrow \quad \angle 60^\circ &= \frac{(1+j)(3+j) - (1-j)(1-j)}{1-j} V_0 \\ &= \frac{3+j+6j-2 - (1-2j-1)}{1-j} V_0 \\ \therefore V_0 &= \frac{\sqrt{2} \angle -45^\circ}{1+j} \angle 60^\circ = \frac{\sqrt{2} \angle -45 \angle 60^\circ}{\sqrt{2} \angle 45.66^\circ} \\ &= 0.78 \angle -68.66^\circ \Rightarrow V_0(t) = 0.78 \cos(5t - 68.66^\circ) \end{aligned}$$

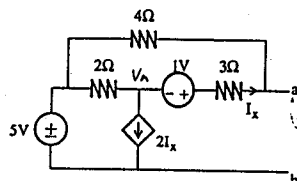- 4) Find the Norton equivalent of the following circuit looking into the terminals a and b. 6 marks



$$V_{oc} = \frac{5 - V_a}{2} = 2I_x + I_x = 3I_x \quad (1)$$

$$\frac{V_A + 1 - V_{OC}}{2} = I_x$$

$$\Rightarrow \frac{f - V_a}{2} = V_a + 2 - V_{oc} \Rightarrow f - V_a = 2V_a + 2 - 2V_{oc}$$

$$\Rightarrow 2V_{OC} = 3V_A - \quad (2)$$

$$\frac{5 - V_{oc}}{4} = -I_x = -\frac{1}{3}(V_{A+1} - V_{oc})$$

$$15 - 3V_{oc} = -4V_a - 4 + 4V_{oc}$$

$$\Rightarrow \quad \uparrow V_{oc} = 19 + 4V_a \quad - (3)$$

$$7V_{oc} = 19 + 4\left(\frac{2}{3}V_{oc} + 1\right) = \frac{8}{3}V_{oc} + 23$$

$$\Rightarrow \frac{13}{3} V_{oc} = 23$$


$$V_{oc} = \frac{3 \times 23}{13} = \frac{69}{13} = 5.3 \text{ V}_{\#}$$

$$\frac{V_a}{2} + 3\left(\frac{V_a - V_o}{3}\right) = 0 \quad \frac{V_a}{2} + V_a - V_o = 0$$

$$\Rightarrow V_o = \frac{3}{2}V_a$$

$$1 = \frac{V_o}{4} + \frac{V_o V_o}{3} = \frac{V_o}{4} + \frac{V_o}{3} - \frac{2}{1} V_o$$


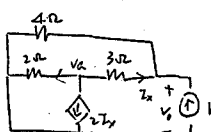
$$\Rightarrow V_o = 2.77 \Rightarrow R_{in} = 2.77 \Omega$$



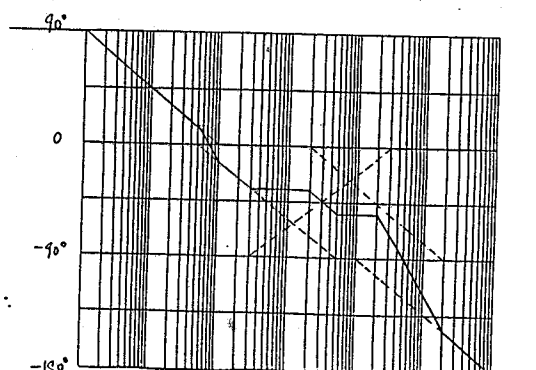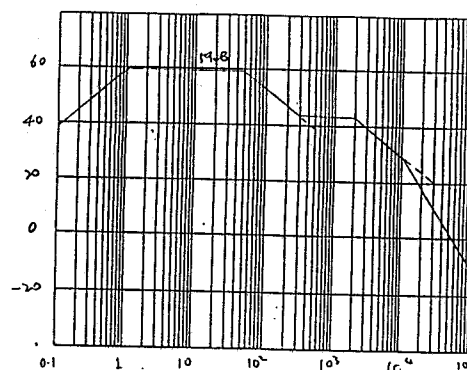- 5) Sketch the Bode plots of the following transfer function. 8 marks

$$H(s) = \frac{3 \times 10^9 (s + 300)}{(s+1)(s+50)(s+2000)(s+10000)} = \frac{3 \times 10^9 s (1 + \frac{s}{300}) 300}{(1+s)(1+\frac{s}{50})(1+\frac{s}{2000})(1+\frac{s}{10000})} \rightarrow 2 \times 10^{10} \times 10^4$$


$$= \frac{900s(1 + \frac{s}{300})}{(1+s)(1+\frac{s}{50})(1+\frac{s}{2000})(1+\frac{s}{10000})} \quad 900 \Rightarrow 19 \text{ dB}$$



$I_{L_2} = \frac{5.3}{2.77} = 1.92 \text{ A}$

- a) Negative resistance can be obtained by using active devices.
For the circuit shown below, compute the negative resistance $R_{in} = V_i/I_i$.

4 marks

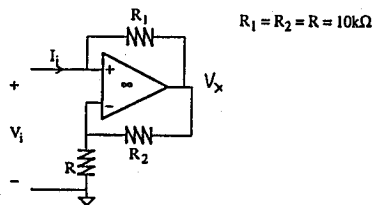

$$R_1 = R_2 = R = 10k\Omega$$

$$V_- = \frac{R}{R+R_2} V_x = V_i$$

$$I_i = \frac{V_i - V_x}{R} = \frac{V_i - \frac{R+R_2}{R} V_i}{R}$$

$$I_i = -\frac{R_2}{R} \frac{1}{R} V_i$$

$$R_{in} = \frac{V_i}{I_i} = -\frac{R}{R_2} R$$

$$= -10k\Omega$$

9

- 6b) The op-amp is not ideal, and $A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$, with $A_0 = 500$, and $\omega_0 = 2000$.

8 marks

Compute the pole and zero of the negative impedance.

$$V_- = \frac{R}{R+R_2} V_x$$

$$I_i = \frac{V_i - V_x}{R_1}$$

$$V_x = A(V_i - V_-) \Rightarrow V_x = A V_i - \frac{A R}{R+R_2} V_x$$

$$V_x (1 + A \frac{R}{R+R_2}) = A V_i$$

$$I_i = \frac{V_i - \frac{A}{1 + A \frac{R}{R+R_2}} V_i}{R_1} = \frac{1}{R_1} (1 - \frac{A}{1 + A \frac{R}{R+R_2}}) V_i$$

$$\frac{V_i}{I_i} = R_{in} = \frac{R_1}{1 - \frac{A}{1 + A \frac{R}{R+R_2}}} = \frac{R_1 (1 + A \frac{R}{R+R_2})}{1 + A \frac{R}{R+R_2} - A}$$

$$= \frac{R_1 A \frac{R}{R+R_2} (1 + \frac{1}{A} \frac{R+R_2}{R})}{1 - \frac{R_2}{R+R_2} A} = \frac{R_1 A}{R+R_2} \frac{(1 + \frac{1}{A} (1 + \frac{R_2}{R}))}{1 - \frac{R_2}{R+R_2} A}$$

$$= -\frac{R_1}{R_2} R \frac{1 + \frac{1 + \frac{R_2}{R}}{A} (1 + \frac{R_2}{R})}{1 - \frac{1 + \frac{R_2}{R}}{A} (1 + \frac{R_2}{R})}$$

$$\approx -\frac{R_1}{R_2} R \frac{1 + (1 + \frac{R_2}{R}) \frac{5}{10^4}}{1 - (1 + \frac{R_2}{R}) \frac{5}{10^4}}$$

$$\omega_0 = 2000$$


$$\text{pole } s_p = -\frac{\omega_0}{1 + \frac{R_2}{R}} = -\frac{10^4}{2} = -5 \times 10^3 \text{ rad/s}$$

$$\text{zero } s_z = +\frac{\omega_0}{1 + \frac{R_2}{R}} = +5 \times 10^3 \text{ rad/s}$$

10

- 7a) Let the output of the op-amp $v_o(0)$ be at 10V initially, and $v_c(0) = -5V$. Assume ideal op-amp with power supply of +10V and -10V. Calculate the time needed for v_o to change state.
Hint: Perform transient analysis (with solution in the form of $k_1 + k_2 e^{-t/\tau}$). Note that $v_o \neq v_-$, except at change of state.

8 marks

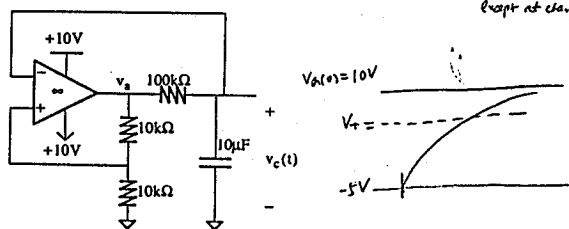

$$v_o(0) = 10V \Rightarrow V_+ = 5V$$

Now, capacitor charges towards 10V. i.e.

$$v_c(t) = k_1 + k_2 e^{-t/\tau}$$

$$\tau = RC = 100k \times 10\mu = 1 \text{ sec.}$$

$$v_c(0) = -5 \Rightarrow k_1 + k_2 = -5$$

$$v_c(\infty) = 10 \Rightarrow k_1 = 10 \Rightarrow k_2 = -15$$

$$\therefore v_c(t) = 10 - 15 e^{-t}$$

$$\text{Op amp change state when } v_c(t) = 5V \Rightarrow 5 = 10 - 15 e^{-t}$$

$$\Rightarrow e^{-t} = \frac{1}{3} \quad t_1 = 1.0995$$

- b) Let t_1 be the time the op-amp changes its state. What are $v_o(t_1)$ and $v_c(t_1)$?

4 marks

at t_1 , op-amp changes state,

$$\therefore v_o(t_1) = -10V$$


$$\text{and } v_c(t_1) = 5V$$

11

- 7c) Calculate the time elapsed for the op-amp to change to its initial state.

4 marks

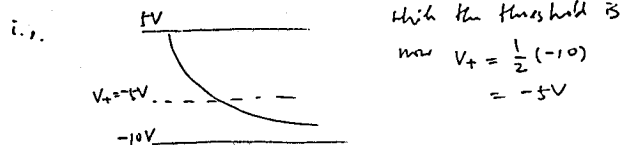now, the capacitor starts to discharge towards -10V.



$$v_c(t) = k_1 + k_2 e^{-t/\tau} \quad \tau = 1$$

$$v_c(0) = 5V \Rightarrow k_1 + k_2 = 5$$

$$v_c(\infty) = -10 \Rightarrow k_1 = -10 \Rightarrow k_2 = 15$$

$$\therefore v_c(t) = -10 + 15 e^{-t}$$


$$v_c(t_1) = -5 = -10 + 15 e^{-t_1}$$

$$\Rightarrow \frac{1}{3} e^{-t_1}$$

$$\Rightarrow t_1 = 1.0995$$

- 7d) The circuit of (7) is an oscillator. From (7a) and (7c), calculate the oscillation frequency.

4 marks

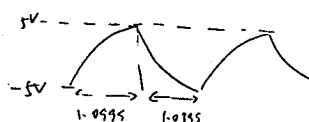


$$\Rightarrow f = \frac{1}{T} = \frac{1}{2.199 + 1.099} = 0.455 \text{ Hz}$$

12

- a) An NMOS transistor is used to construct a voltage regulator. With an ideal op-amp, calculate the voltage at the gate V_g .

6 marks

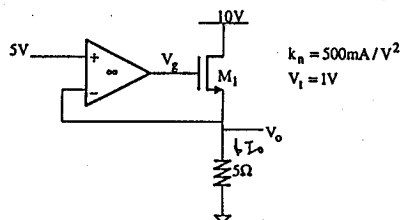

Ideal op-amp $\Rightarrow V_o = V_- = V_+ = 5V$.

$$I_o = \frac{5V}{5\Omega} = 1A \Rightarrow I_d = 1A.$$

Assume M_1 in saturation, $I_d = 1A = \frac{1}{2}(0.5)(V_{gs} - V_t)^2$

$$\Rightarrow (V_{gs} - V_t)^2 = 4$$

$$\Rightarrow V_{gs} - V_t = 2$$

$$\Rightarrow V_g - V_o - 1 = 2$$

$$\Rightarrow V_g = 2 + 5 + 1 = 8V$$

check: $V_{gs} - V_t = 2$, $V_{ds} = 10 - 5 = 5V$

$\therefore V_{gs} - V_t < V_{ds} \Rightarrow$ saturation.

- b) Is the NMOS transistor operating in the saturation or linear region?

2 marks

Saturation

- 8c) Now, the op-amp is not ideal, but with a DC gain of $A_o = 500$. Assume V_o is approximately 5V, recalculate V_g , and thus obtain a more accurate V_o .

4 marks

$$\text{For } A_o = 500,$$

$$V_g = (5 - V_-)500 = 8$$

$$\Rightarrow 5 - V_- = \frac{8}{500} = 16m$$

$$\Rightarrow V_- = 5 - 16m$$

$$= 4.984V$$

$$V_o = V_- = 4.984V$$

- 8d) Next, with the above non-ideal op-amp, the load resistor is changed to 2.5Ω . Calculate the new V_o .

6 marks

$$\text{Assume } V_o = 5V, \quad I_d = 2A = \frac{1}{2}\left(\frac{1}{2}\right)(V_{gs} - V_t)^2$$

$$\Rightarrow V_{gs} - V_t = 2\sqrt{2} = 2.828$$

$$\Rightarrow V_g - 5 - 1 = 2.828$$

$$\Rightarrow V_g \approx 8.828$$

$$= (5 - V_-)500$$

$$\Rightarrow V_- = 5 - \frac{8.828}{500} = 5 - 0.0177 = 4.9813V$$

- 8e) With the result obtained in (8c) and (8d), calculate the load regulation $\Delta V_o / \Delta I_o$.

2 marks

$$\frac{\Delta V_o}{\Delta I_o} = \frac{4.984V - 4.9813V}{1A - 2A} = -2.7mV/A$$